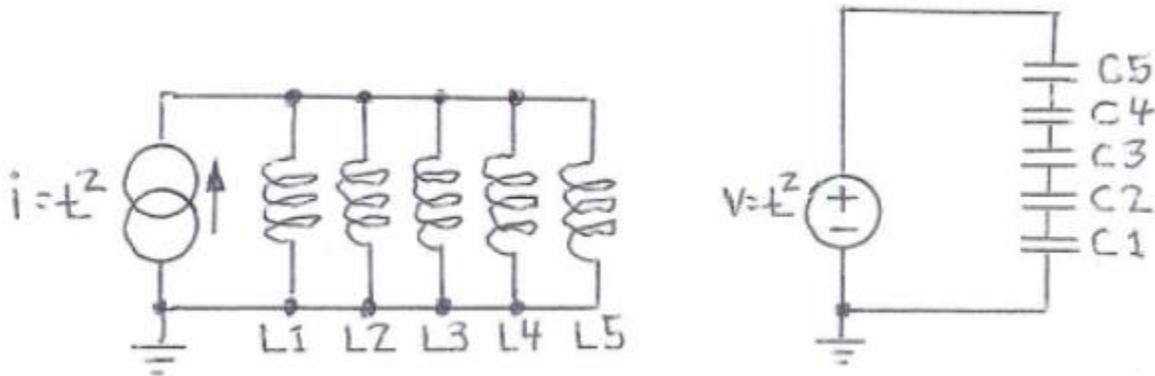


## Circuit Challenge 6

Consider the two circuits shown below.



### The Situation

James has 5 inductors and a current source. Lisa has 5 capacitors and a voltage source. The inductor and capacitor values are as listed in the table below.

Inductor	Value	Capacitor	Value
L5	$8\mu\text{H}$	C5	$8\mu\text{F}$
L4	$8\mu\text{H}$	C4	$8\mu\text{F}$
L3	$4\mu\text{H}$	C3	$4\mu\text{F}$
L2	$2\mu\text{H}$	C2	$2\mu\text{F}$
L1	$1\mu\text{H}$	C1	$1\mu\text{F}$

James wants to know when ( $t=?$ ) 1 Ampere will be flowing in  $L_1$ , and he wants to know what the voltage will be across  $L_1$  at that time.

Lisa wants to know when ( $t=?$ ) 1 Volt will appear on  $C_1$ , and she wants to know how much current will be flowing in  $C_1$  at that time.

### The Challenge

Determine the times, the voltage, and the current.

Compare your calculations with what you find by scrolling down to the author's analysis.

## Analysis for Challenge 6

### James' Circuit

$L_2$ ,  $L_3$ ,  $L_4$ , and  $L_5$  have a combined parallel inductance of  $1\mu\text{H}$  (equivalent to  $L_1$ ). Thus, half the input current will always be flowing in  $L_1$ , and we can write

$$i_{L1} = t^2/2$$

Then, we solve for  $t$  when  $i_{L1}$  is 1 Ampere, as follows:

$$1 = t^2/2$$

$$t^2 = 2$$

$$t = \sqrt{2} \text{ seconds}$$

The voltage on  $L1$  is found using the following relationship:

$$v_{L1} = L_1 di/dt$$

For  $L_1$ ,  $di/dt = t$  Amperes/sec. Therefore we can write

$$v_{L1} = L_1 t(\text{A/sec})$$

In this case  $t = \sqrt{2}$ . Thus,

$$v_{L1} = 1\mu\text{H}(\sqrt{2})(\text{A/sec})$$

$$v_{L1} = (\sqrt{2})\mu\text{V} \leftarrow \text{voltage on } L_1 \text{ when the current in } L_1 \text{ is 1 Ampere}$$

### Lisa's Circuit

$C_2$ ,  $C_3$ ,  $C_4$ , and  $C_5$  have a combined series capacitance of  $1\mu\text{F}$  (equivalent to  $C_1$ ). Thus, half the input voltage will always appear on  $C_1$ , and we can write

$$v_{C1} = t^2/2$$

Then, we solve for  $t$  when  $v_{C1} = 1$  Volt

$$1 = t^2/2$$

$$t^2 = 2$$

$$t = \sqrt{2} \text{ seconds}$$

The current in  $C_1$  is found using the following relationship:

$$i_{C1} = C_1 dV/dt$$

For  $C_1$ ,  $dV/dt = t$  volts/sec. Therefore we can write

$$i_{C1} = C_1 t (\text{V/sec})$$

In this case  $t = \sqrt{2}$ . Thus,

$$i_{C1} = 1 \mu\text{F} (\sqrt{2}) (\text{V/sec})$$

$$i_{C1} = (\sqrt{2}) \mu\text{A} \quad \leftarrow \text{current in } C_1 \text{ when the voltage on } C_1 \text{ is } 1\text{V}$$

### **Did You Notice?**

Both input sources have finite slopes at  $t=0$ .

- If  $i$  had instantly stepped from 0 to some non-zero value,  $L di/dt = \infty$
- If  $v$  had instantly stepped from 0 to some non-zero value,  $C dv/dt = \infty$